

#Home work 4 2025.04.16(Due: 04.25, 13:20)

```

/* Using 16 nm ADFP FiFFT devices with VDD= 0.8 V, FF process
corner and medium Vt CMOS process*/
/*Rise time and fall time of input signals and clock are all 0.01ns (0V-
0.8V)*/

```

1. A 6-bit one stage pipelining ripple adder as shown at Fig.4.1(a) is designed with Fully Complementary Static Logic Gate for the 1-bit FA as shown at Fig4.1(b) and the D-register as shown at Fig.4.1(c). Input signals are A[5:0], B[5:0] and Cin which are provided by a unit size inverter. Outputs are Cout@Sum [6:0] with loading of 4 unit size inverters (FO4) connected in parallelism. **You shall provide SPICE simulation results of timing and power waveforms.**
- (1) Try your best to design the fastest adder without pipelining registers. First, show your block diagrams in terms of the 1-bit Full-Adder(FA). Second, show the circuit schematic of each block. Use logic effort concepts (you do not have to write down the procedure) to design transistor widths (in table form). **Describe your design concept.** (40%)
- (2) Based on the design of (1), run SPICE to find the the propagation delay time (with pattern from 000001111110 to 000001111111 (A[5:0]@B[5:0]@Cin). Determine the minimum clock cycle time with the delay time estimated by SPICE. (20%)
- (3) Run SPICE to get the average, peak and leakage power dissipation and energy/bit, respectively of this adder with loading (FO4) when working at the maximum working frequency. (20%)
- (4) Add one pipelining stage using the designed D register (Fig.4.1(b)) into the 4-bit ripple adder as shown at Fig.4.1(a). Run SPICE to find the the propagation delay time (with pattern from 00001111110 to 00001111111 (A[5:0]@B[5:0]@Cin) between pipelining stages to determine the maximum working frequency of the clock with the delay time estimated by SPICE. (20%)

 


Fig. 4.1(a) Pipeline design of 4 bit adder

 


Fig.4.1 (b) Dynamic D register .

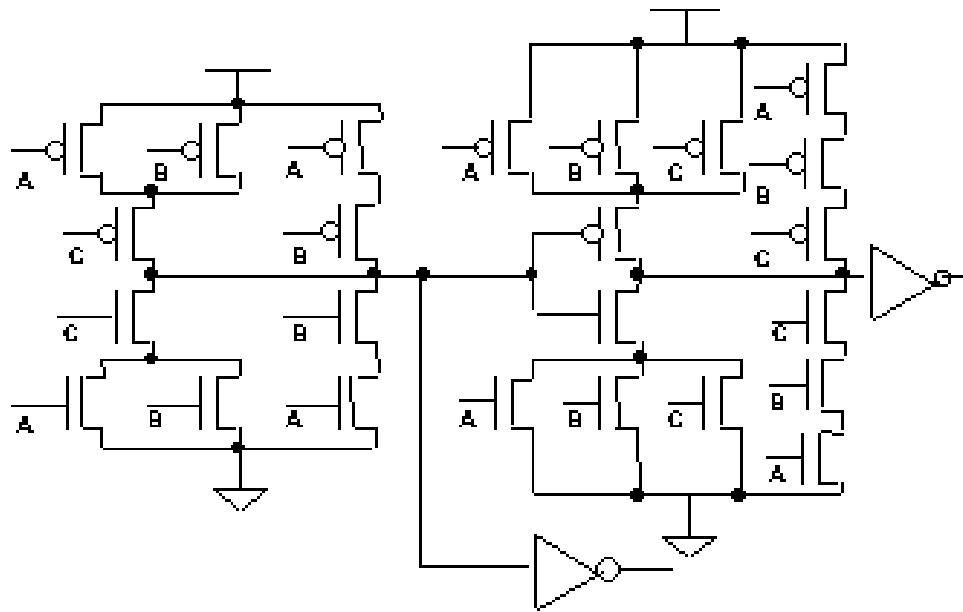


Fig.4.1 (c) 1-bit static Full adder.

*/*You should provide the SPICE input description, timing and power waveforms*/*