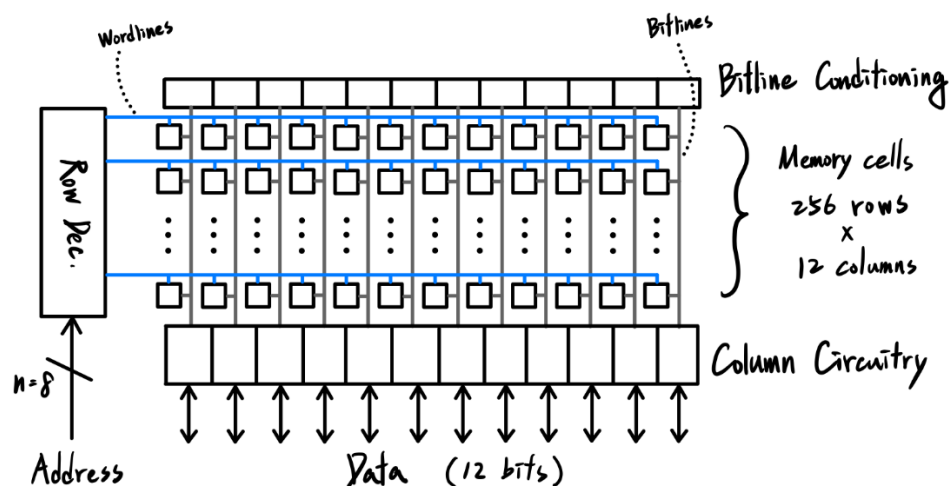


Digital Integrated Circuits homework 6 電子所 陳柏翔 313510156

1. Design an embedded SRAM contains **256 x 12-bit** words.


(a) **Plan A:** Draw the memory array architecture like that shown in Fig.12.2(a) of class note page 2. Mark necessary inputs, outputs and signals.



 (b) **Plan B:** If it is physically arranged in a square fashion like that shown in Fig.11.2 (b) with proper k address bits used in the column decoder, draw the memory architecture. Indicate the number of inputs to each column multiplexer. Mark necessary inputs, outputs and signals.

先找出最接近正方形分布的 rows \times columns :

- Rows: $\log_2 \sqrt{256 \times 12} = 5.7925 \approx 6 \rightarrow$ 設 Number of rows = $2^6 = 64$
- Columns: $256 \times 12 \div 64 = 48 \rightarrow$ 設 Number of columns = 48



(c) List in table form for Design A and B of the following items:

- (i) The number of Wordline and the number of memory cell in a Wordline.
- (ii) The number of Bitline and the the number of memory cell in a Bitline.

Table of (i)	Plan A	Plan B
Wordline	256	64
Memory cells	12	48

Table of (ii)	Plan A	Plan B
Bitline	12	48
Memory cells	256	64

(d) Why Plan B is better than A? Compare from Area (the decoder size), Speed (Worldline and Bitline loading) and Power point of view. You shall describe the factors and facts.

1. **Area (Decoder size):**

- Plan A: row decoder 需要 $8 \times$ Inverters + $256 \times$ 8-input AND Gate.
 - Plan B: row decoder 需要 $6 \times$ Inverters + $64 \times$ 6-input AND Gate,
column decoder 需要 $2 \times$ Inverters + $4 \times$ 2-input AND Gate.
- ⇒ Plan B所需的Gate數量與面積都遠小於Plan A。

2. **Speed:**

	Plan A	Plan B
Wordline loading	12	48
Bitline loading	256	64

- Wordline loading: Plan A < Plan B (Plan A好一些)
 - Bitline loading: Plan A >> Plan B (Plan B好很多)
- ⇒ 對於Critical path而言，Plan A需走256個memory cells (loading較大)，遠大於Plan B的64個memory cells。


3. **Power:** $P = fCV^2 \propto C$

- Decoder power: Plan A所需Gate數遠大於Plan B，因此Dynamic power會較大。
- Wordline power: Plan A的Wordline loading較Plan B來得小，因此Plan A的switching power會較Plan B小。
- Bitline power: Plan A的Bitline loading(=256)較Plan B(=64)大很多，會有更大的電容要充放電，因此switching power和leakage power都會較大。

總結：在Area與Speed方面都是Plan B較佳，而Power方面除了Wordline loading的面向上Plan A會較佳，其他都是Plan B較佳，因此整體而言Plan B是較好的設計。


- (e) Propose two designs of **Plan B** (i) **precoding for row decoder** and (ii) **Hierarchical wordline**. You shall describe the factor and facts that these two methods can reduce area and/or delay time.

(i) **Precoding:**

 

透過Precoding，可以利用邏輯共用的方式，省去大部分繁冗的NAND gates以有效reduce area。同上課講義所述，由於路徑上與原先的設計一樣需要經過INV-NAND-NOR或者NAND-NOR，因此path effort不改變、delay time也不會有太多的變化，而此設計優化的重點不在速度上。

(ii) **Hierarchical wordline:**

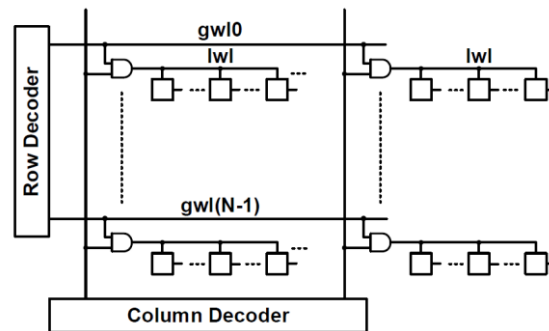

在Hierarchical wordline的方法中，將wordline分成global wordline(gwl)與local wordline(lwl)，這樣的做法取代了原先直接看到的大量memory cells，而是只在global層只看到AND gate的輸入端loading、在local層看到少量的memory cells的loading，這樣能夠降低看到的電容大小，以減少RC delay來讓電路速度提升。並且由於只有被local wordline啟動的bitlines才會動作，所以功耗也能有效下降。