

# Digital Integrated Circuits

#Home Work 8      2025.05.28 (Due:2025.06.04, 15:30)

Consider the circuit in Fig.8. Modules A and B have a delay of 20ns and 30 ns at 1.0 V ( $V_{dd}$ ), and switch 20 pF and 35 pF (C) respectively. All the buses in Fig.8 are 16 bits. The register has a 0.4 ns delay and switches 0.05 pF. The clock rate of Fig.7 is thus  $1/(50 \text{ ns})$  and the power dissipation is  $P_0$ . The power dissipation can be estimated by  $P = C \cdot V_{dd}^2 \cdot F$  and the delay with respect to  $V_{dd}$  can be approximated by  $k/(V_{dd} - V_t)$  with  $V_t$  equals 0.3 V.  $k$  is a constant and is different for A and B. You can use the information of delay time,  $V_{dd}$  and  $V_t$  to calculate  $k$ .

- (a) Adding a pipeline register between A and B allows for reduction of the supply voltage (A and B can use different  $V_{dd}$ ) while maintaining throughput ( $P_1$ ). Show the block diagram, explain the operation and calculate the power reduction ratio,  $P_1/P_0$  (30%)
- (b) Assume that a 2-to-1 multiplexer has a delay of 0.4 ns at 1.0 V and switches 0.05 pF. Try parallel version with two copies (using two A and B modules) while maintaining data rate ( $P_2$ ). Show the block diagram, explain the operation and calculate power reduction ratio,  $P_2/P_0$ . (30%)
- (c) Try to combine (a) and (b) to design a parallel-pipeline version while maintaining data rate( $p_3$ ). Show the block diagram, explain the operation and calculate power reduction ratio,  $P_3/P_0$  (40%)

